

Advanced Diploma in Engineering / Advanced Diploma in Lift Engineering
Semester 1, 2018-19

Assignment

Programme Code : IT021
Module Code : ENGG4016 / ENGG4039
Course Title : **Electrical and Electronic Principles**
Total Marks : 100 marks
Submission Deadline : 13 Nov 2018

Class : _____

Name : _____


Student ID : _____

Marks

/100


Question 1 a) Find V_o of the following circuit.

(25 marks)

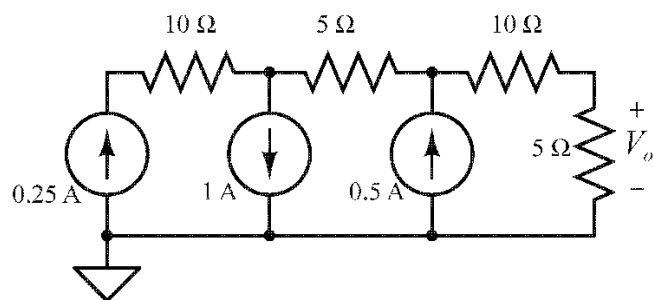


Solution:

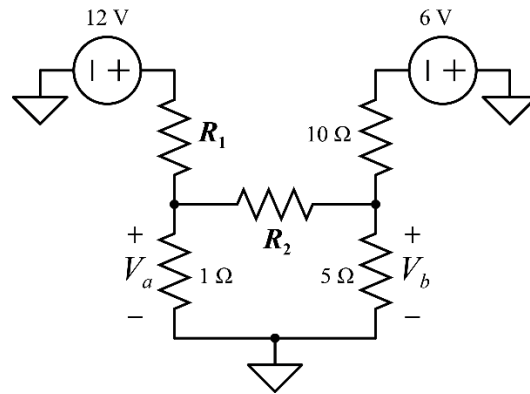- b) Given $V_a = 3.2\text{ V}$ and $V_b = 2\text{ V}$ in the circuit below, find the values of R_1 and R_2 .



Solution:

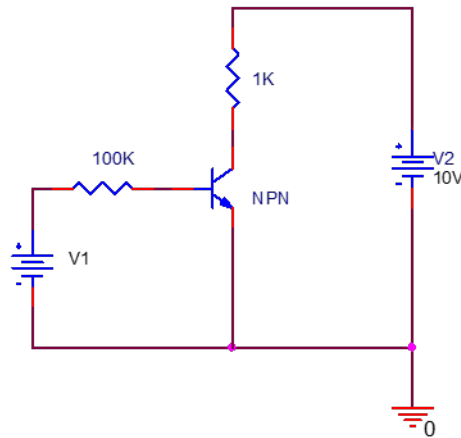
Question 2 The figure below is a BJT transistor amplifier configuration with $\beta = 100$ and $V_{BE} = 0.7V$, where R_B is $100K\Omega$ base resistor. (25 marks)



- What is the collector current and the collector-emitter voltage if transistor is in cutoff state?
- Find the expression of collector current in respect of V .
- What is the saturated current in emitter?
- What happen to the transistor if R_B is being removed with $V = 1V$?
- What is the name of this configuration?


Solution:

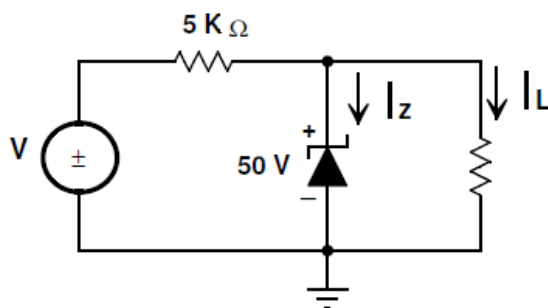Question 3 From the circuit below, determine the range of the voltage source if: $0 \leq I_L \leq 4\text{mA}$ and $2 \leq I_Z \leq 8\text{mA}$ (25 marks)



Solution:

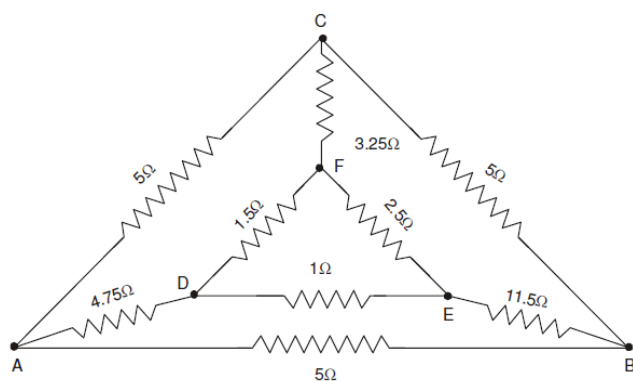- Question 4 Find the resistance between point A and point B in the resistor network below, show your steps clearly. (25 marks)



Solution:

~ End of Assignment ~